



Webinar Series “Lost in Translation”: Selecting the Right Translator

Part 2: Application Examples

June 2022 •

Agenda

Part 1

Technical Requirements

The need for translators

Types of translators

Product Portfolio

Common Interfaces for translators

Link to recorded session:

Part 2

Applications

Specific applications and translator solutions

- The Translator Toolbox
- Translator solutions from actual designs

Special application information

- Autosense translator with push-pull outputs
- Design flexibility with LSF translators
- LSF pullup-up supply case
- NXB with open drain receiver

More resources




01

The Translator Toolbox


Voltage Translators | Decision tree

How to select the right Translator type

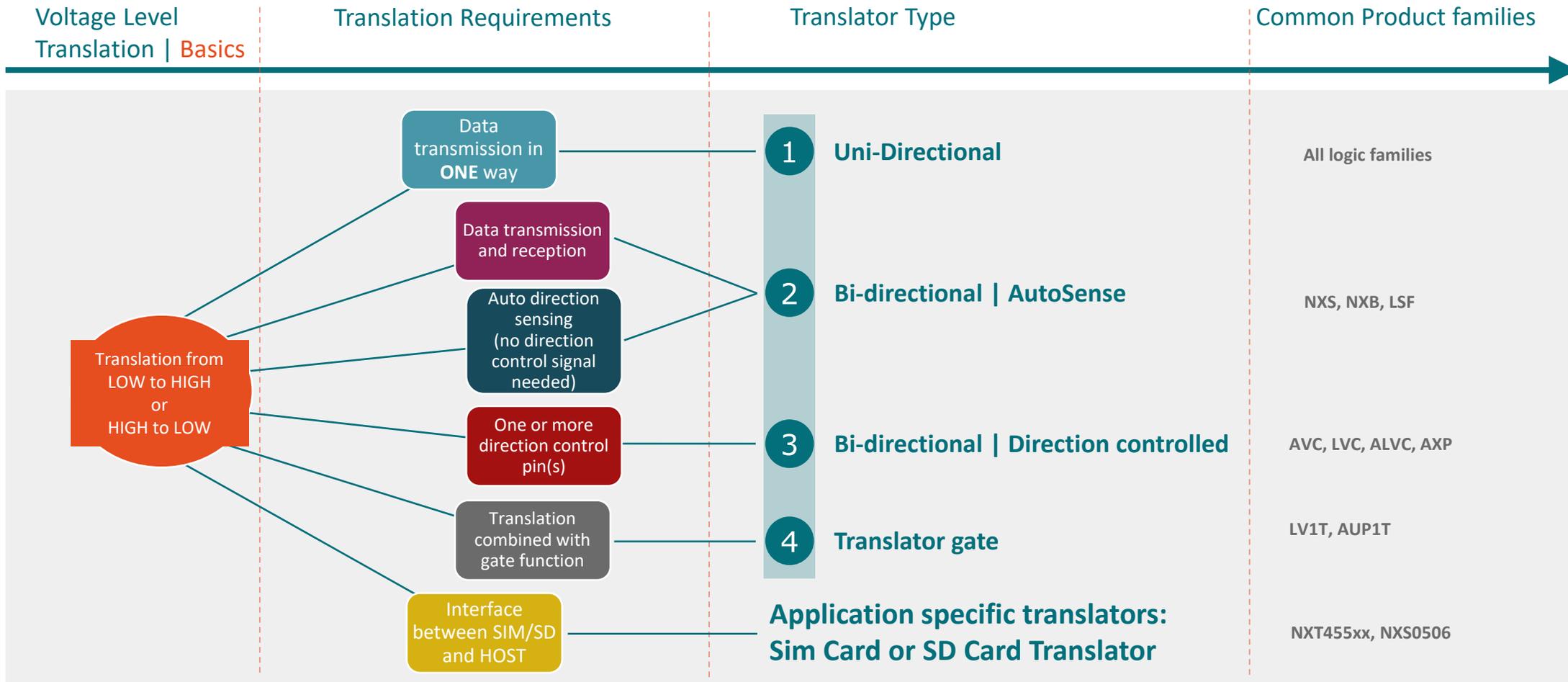

Standard Logic Translators

Embedded Translation

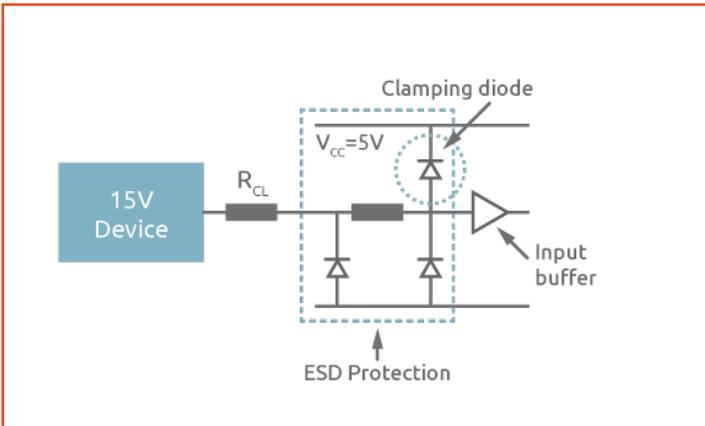

Clamp diode inputs

Advantage:

- Can be used to interface any voltage


Disadvantage:

- Requires external component

Available Families

- HEF4000B*
- HC(T)*
- LV

* HEF4104B, HC4049 & HC4050 only

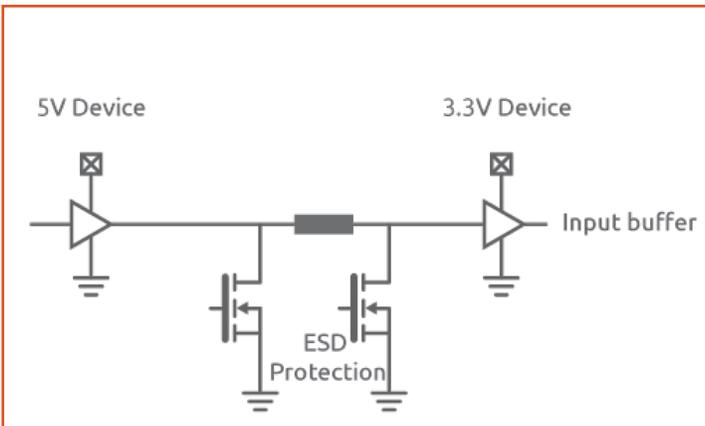

Overvoltage tolerant inputs

Advantage:

- No external components required
- Low system power than the clamp diode solution
- Only one supply voltage needed

Disadvantage:

- Inputs cannot be driven at voltages greater than the recommended maximum value of V_{CC}


Available Families

- AHC
- ALVC*
- ALVT
- AUP
- AVC, LVC
- AXP
- CBTLV(D)
- LV-A

* Non bus-hold only

Logic Translators Techniques

Embedded Translation (cont.)

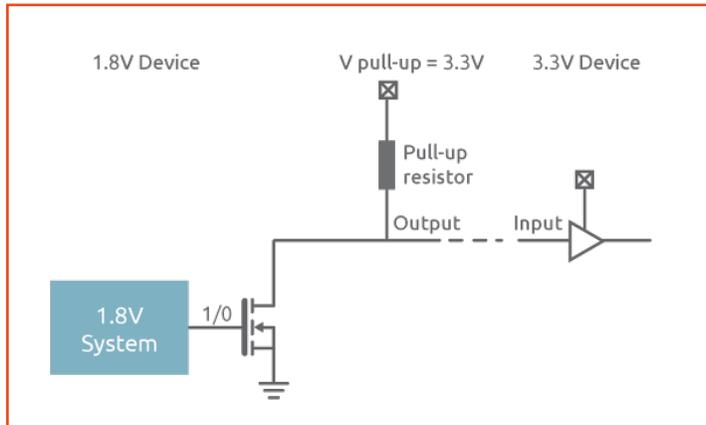

Open-drain outputs

Advantage:


- HIGH to LOW or LOW to HIGH translation
- Can be used in a wired-OR interface

Disadvantage:

- Requires external component
- Additional system power

Available Families

- AHC(T)
- HC(T)
- LVC
- LV
- AUP
- AXP

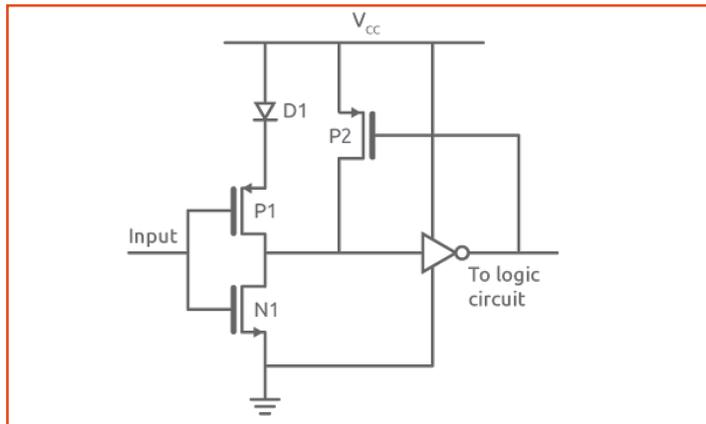

Low-threshold inputs

Advantage:

- No external components required
- Same footprint as standard function

Disadvantage:


- High power dissipation due to ΔI_{CC}

Available Families

- HCT
- AHCT
- LV1T
- LVC
- AUP1T
- AXP

Logic Translators Techniques

Transceivers

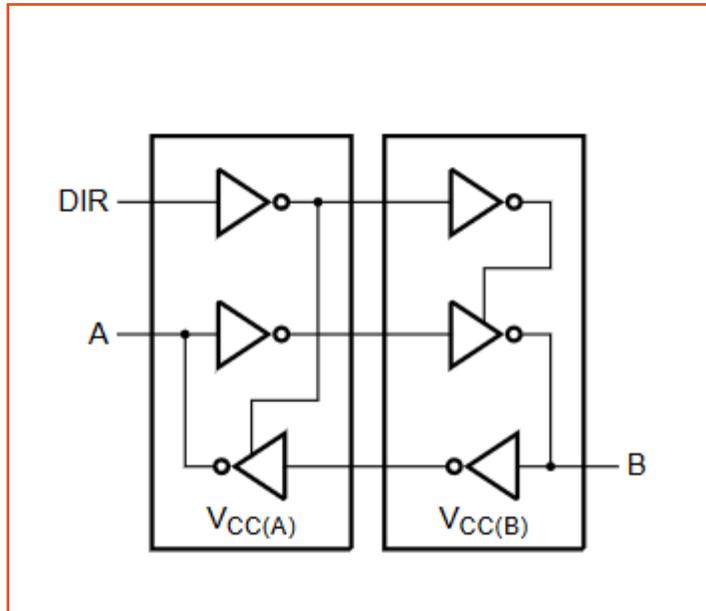

Transceiver (bidirectional Buffer)

Advantage:

- HIGH to LOW or LOW to HIGH translation
- Bidirectional, supports half duplex communication
- Increased voltage translation range compared to single supply

Disadvantage:


- Requires dual supply
- Requires direction pin

Autosense Translators

3 variants

- LSF:
 - pass transistor per channel
 - external pull-up resistors and voltage supply
- NXS:
 - pass transistor with one-shot accelerator for rising edge only
 - internal pull-up circuit
- NXB:
 - push-pull circuit
 - one-shot accelerators for both rising and falling edges

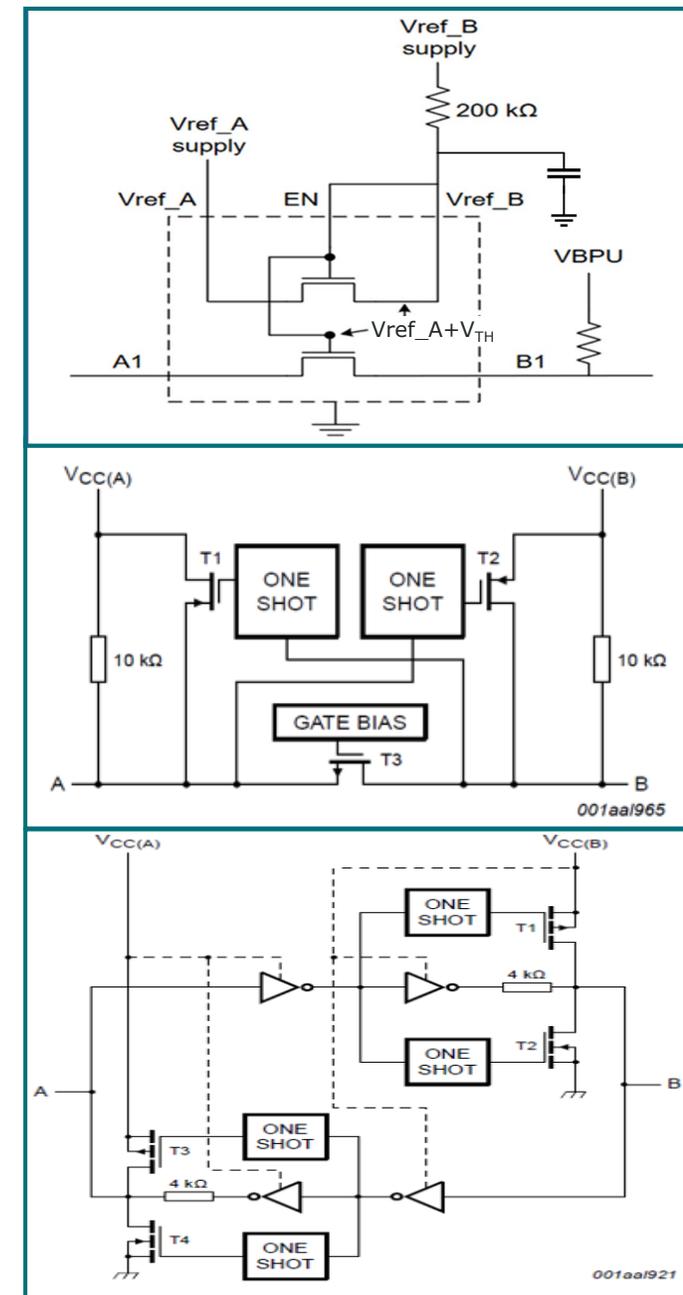More details on Autosense Translators? See our past Webinar at <https://www.nexperia.com/support/on-demand-seminars.html>





02


Applications Solutions

- From actual designs

Translator Example 1:

Application: Garden Tractor control panel

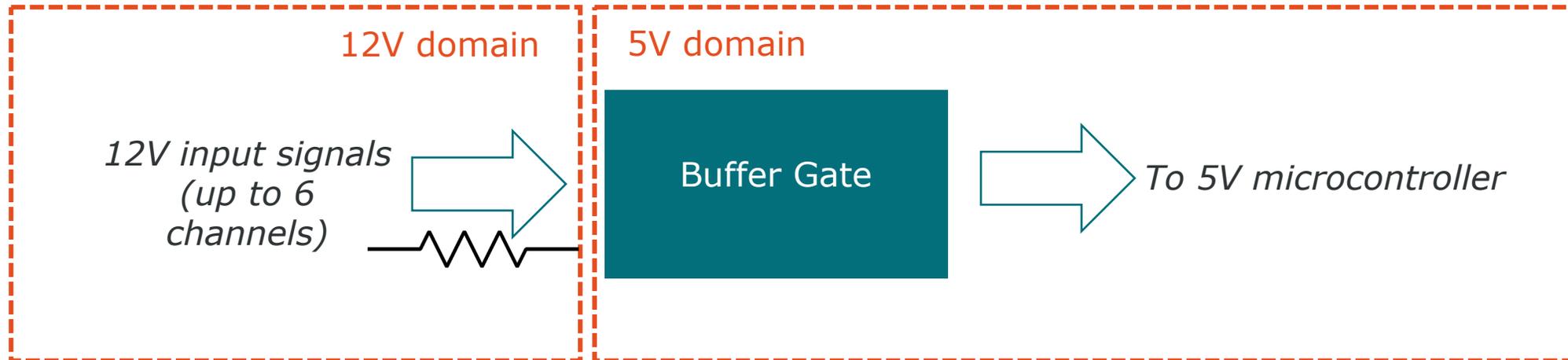Design Issue: 12V status signals from engine to interface to (old) 5V microcontroller



HEF4050 or 74HC4050
(hex buffer) device


$0 < V_{in} < 15V$

Must limit input current
to $< 10mA$
(700 ohm)

Translator Example 2

Application: Industrial controller

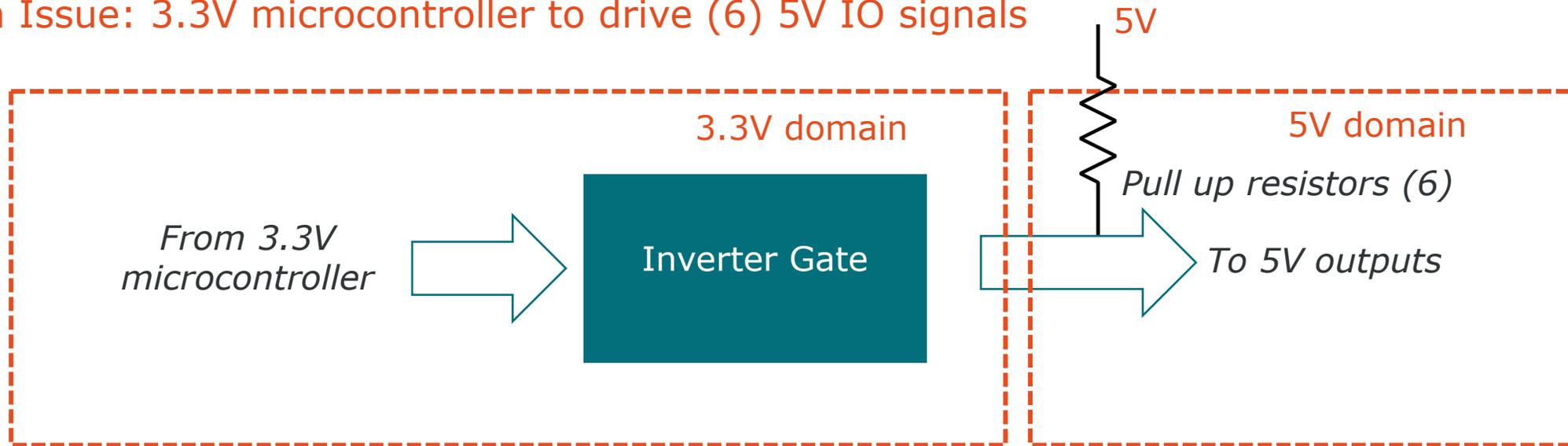Design Issue: 3.3V microcontroller to drive (6) 5V IO signals




74LVC06
(hex inverter open drain)
 $0 < V_{in} < 5.5V$
 $0 < V_{out} < 5.5V$

Translator Example 2 (advanced solution)

Application: Industrial controller

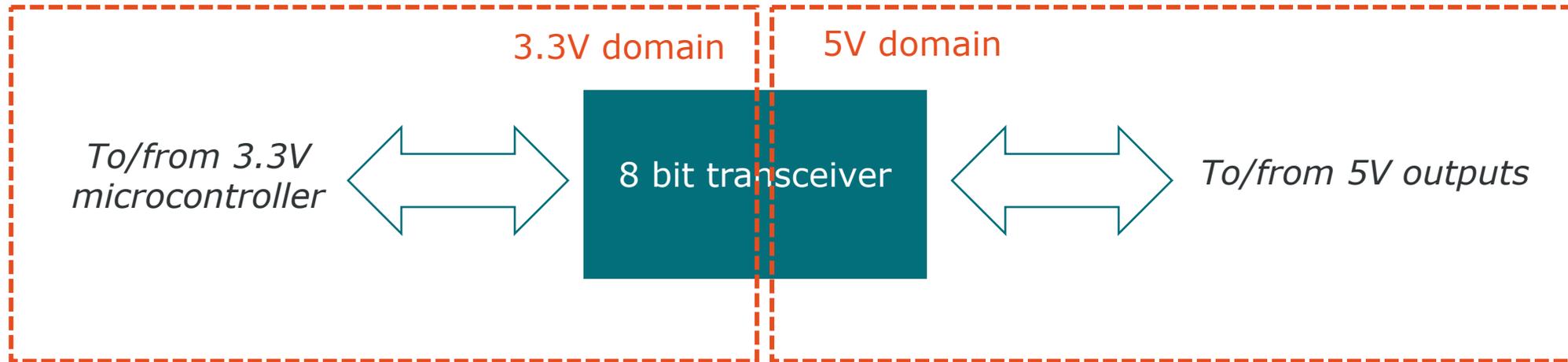Design Issue: 3.3V microcontroller to drive (6) 5V IO signals *bidirectional*





74LVC8T245
(dual supply transceiver)
For bidirectional data

Translator Example 3 (cont.)

Application: Automotive Telematics Control Unit

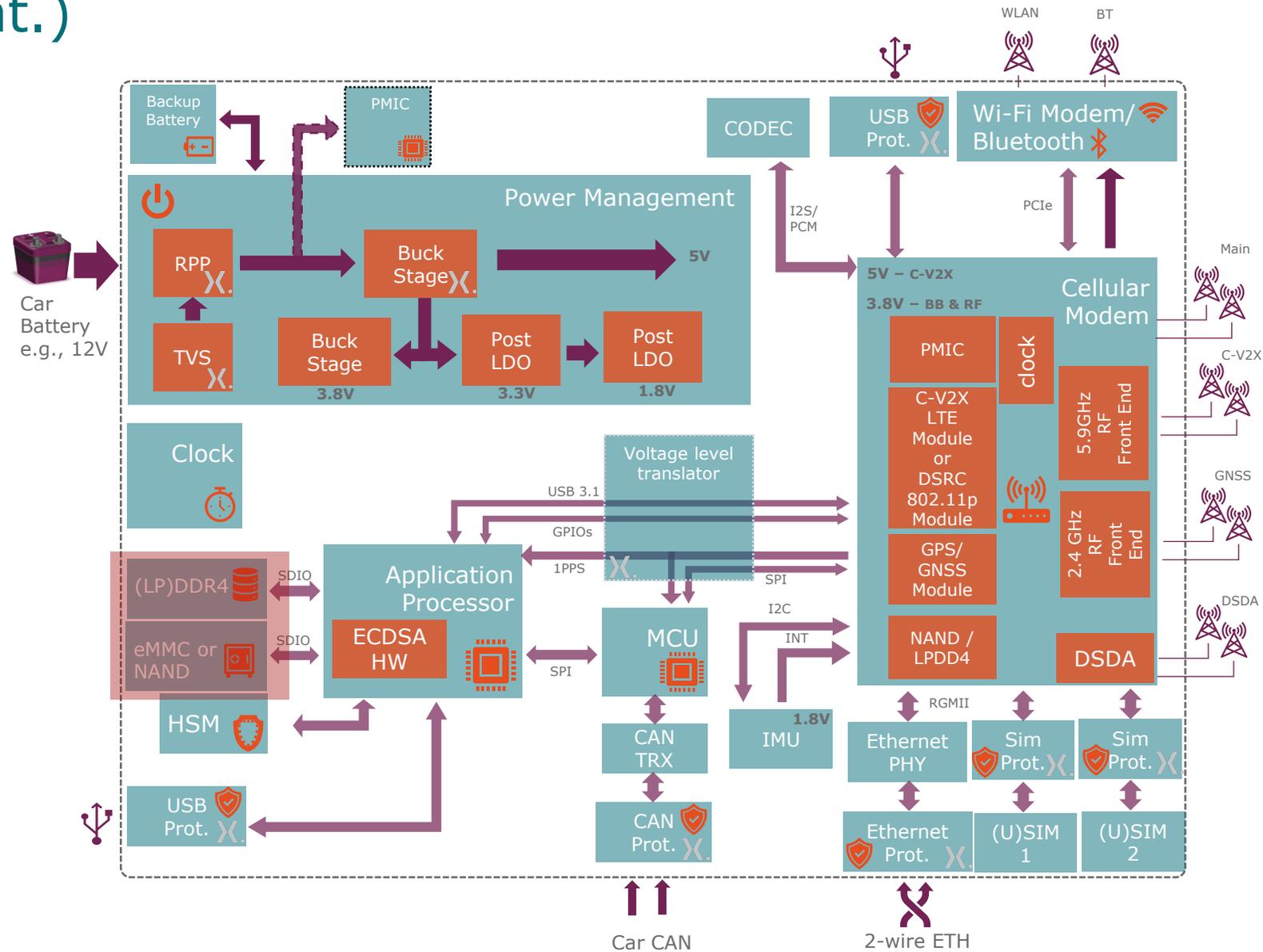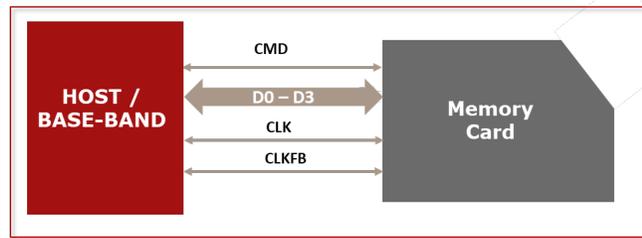- **SD Card Translator**
- NXS0506 – 16 – ball WLCSP





Translator Example 3 (cont.)

Application: Automotive Telematics Control Unit

- **Autosense Translator**

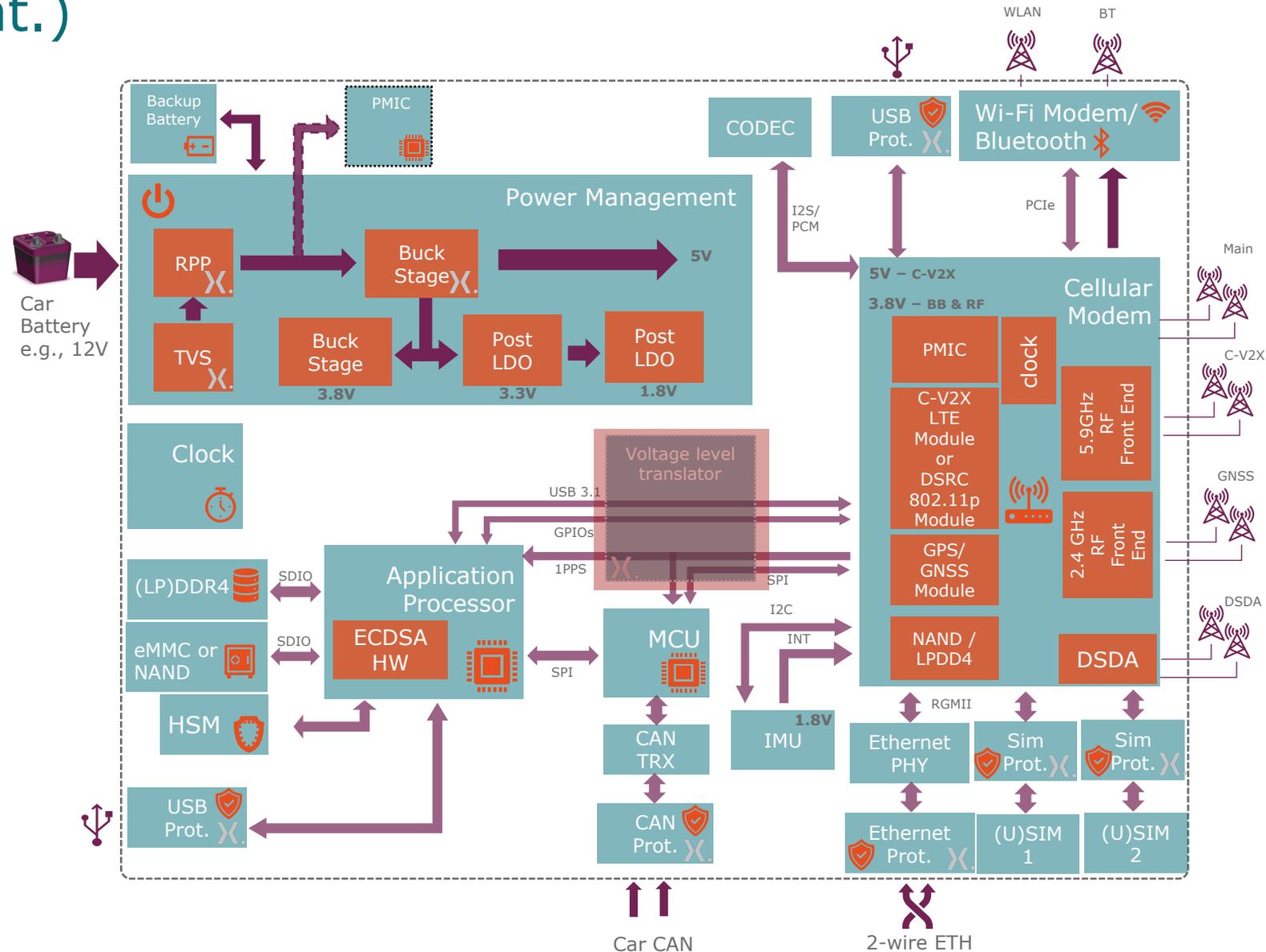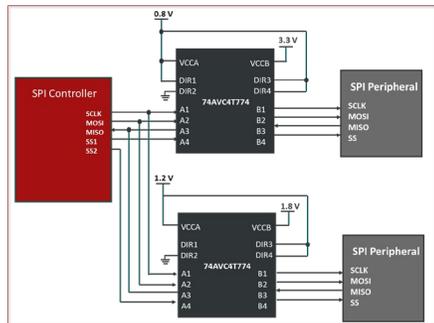
- NXS010x Family
- NXB010x Family
- LSF010x Family
- 74AVC4T3144
- 74AVC4T774




Translator Example 3 (cont.)

Application: Automotive Telematics Control Unit

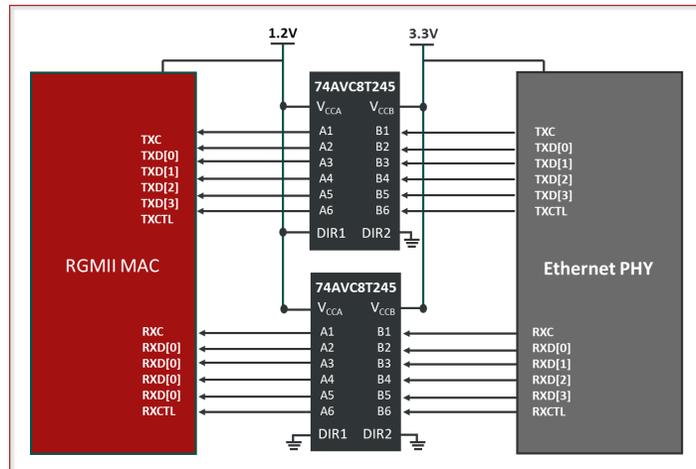- **Translator for RGMII protocol**
- 74AVC8T245 in BQ and PW



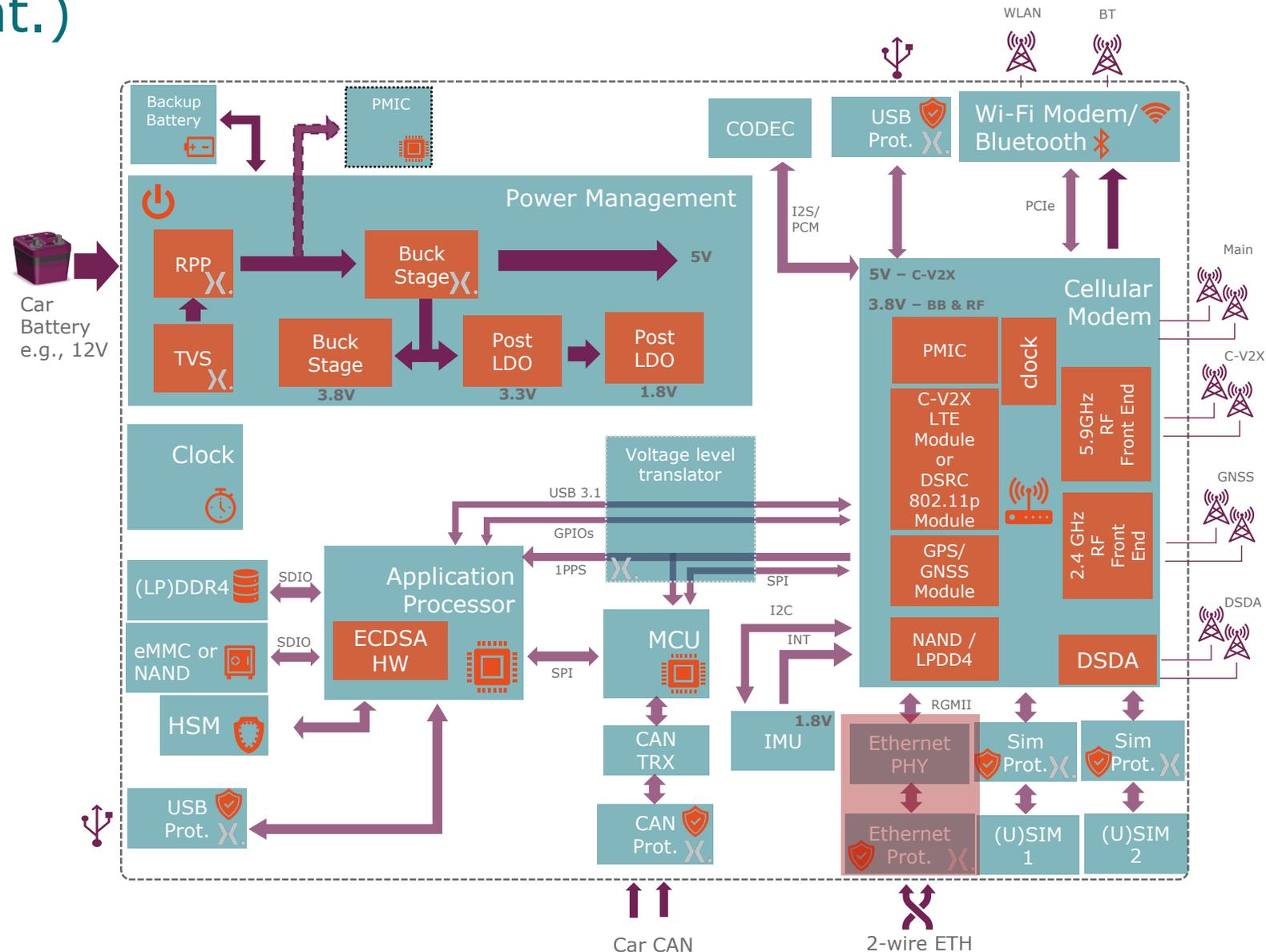RGMII Voltage Translation Using 74AVC8T245



More Customer Applications/Solutions?

Request a copy of our Nexperia Applications Guide:



Contents

Automotive		Industrial	
Active Safety	5	eMeters	37
Analog Gauge Replacements	6	Endpoints	38
Automotive Lighting	7	Energy Devices	39
Battery Management for Electric Vehicles	8	Heating Ventilation Air Conditioning (HVAC)	40
Body Control Module (BCM)	9	Industrial Control	41
Electrical Power Steering (EPS)	10	Motor Control	42
Engine Control Unit (ECU)	11	Point Of Sale (POS)	43
Heating Ventilation Air Conditioning (HVAC)	12	Robotics	44
Infotainment	13	Smart Uninterruptable Power Supply (UPS)	45
On-Board Charger	14	White Goods	46
Passive Safety: Airbag	15	Industrial / Lighting	
Power Block: DC-DC Converter	16	Automatic Lighting Control	48
Sensors: Radar, LIDAR, Camera	17	Office Lighting Fixtures	49
Telematics: e-Call, GPS, V2X	18	Outdoor Street Lighting	50
Computing		Products Suitable for 12 VDC	51
PC Motherboard (Intel Kaby Lake Platform)	20	Retrofit LED bulb	52
SSD Solid State Drives	21	Signage and Display Boards	53
Communication Infrastructure		Industrial / Medical	
Gateways	23	CT Scan Machines	55
Hot Swap Controller	24	ECG/EKG Machines	56
Consumer		Ultrasonic Machines	57
Design House (ODM/JDM/EMS)	26	Portable	
Unmanned aerial vehicles (UAVs) / «Drones»	27	eReader/Tablet PC	59
E-Cigarettes	28	Point-Of-Sale (POS) Reader	60
Gaming	29	USB Type-C Connector	61
Set-Top Box	30	Wearables	62
LED Lighting with Dimming Control	31		
Blood Glucose Meter	32		
Blood Pressure Monitor	33		
Digital Scales	34		
CCTV Security Camera	35		




03

Special Application
use cases


Design flexibility with LSF

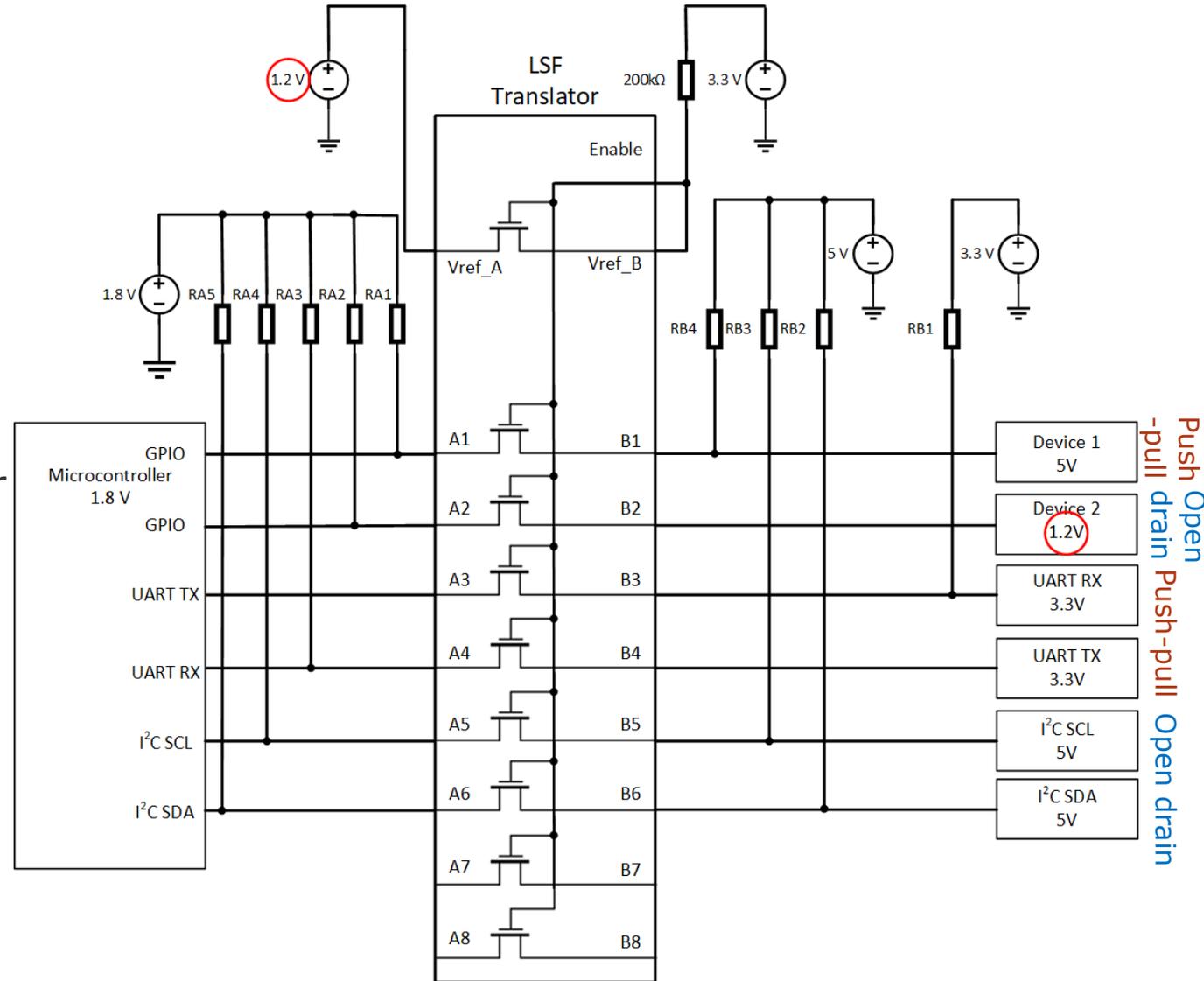- Example case showing an LSF0108 translating between a Microcontroller and various devices
- Interface topologies can be
 - push-pull (UART, Device 1)
 - pull-up needed for the receiver
 - Fix direction or direction control needed to avoid high/low driver conflict, no pull-up for the driver
 - open-drain (I2C, Device 2)
 - Pull-ups needed on both sides
 - No direction control needed, full autosense flexibility



Design flexibility with LSF

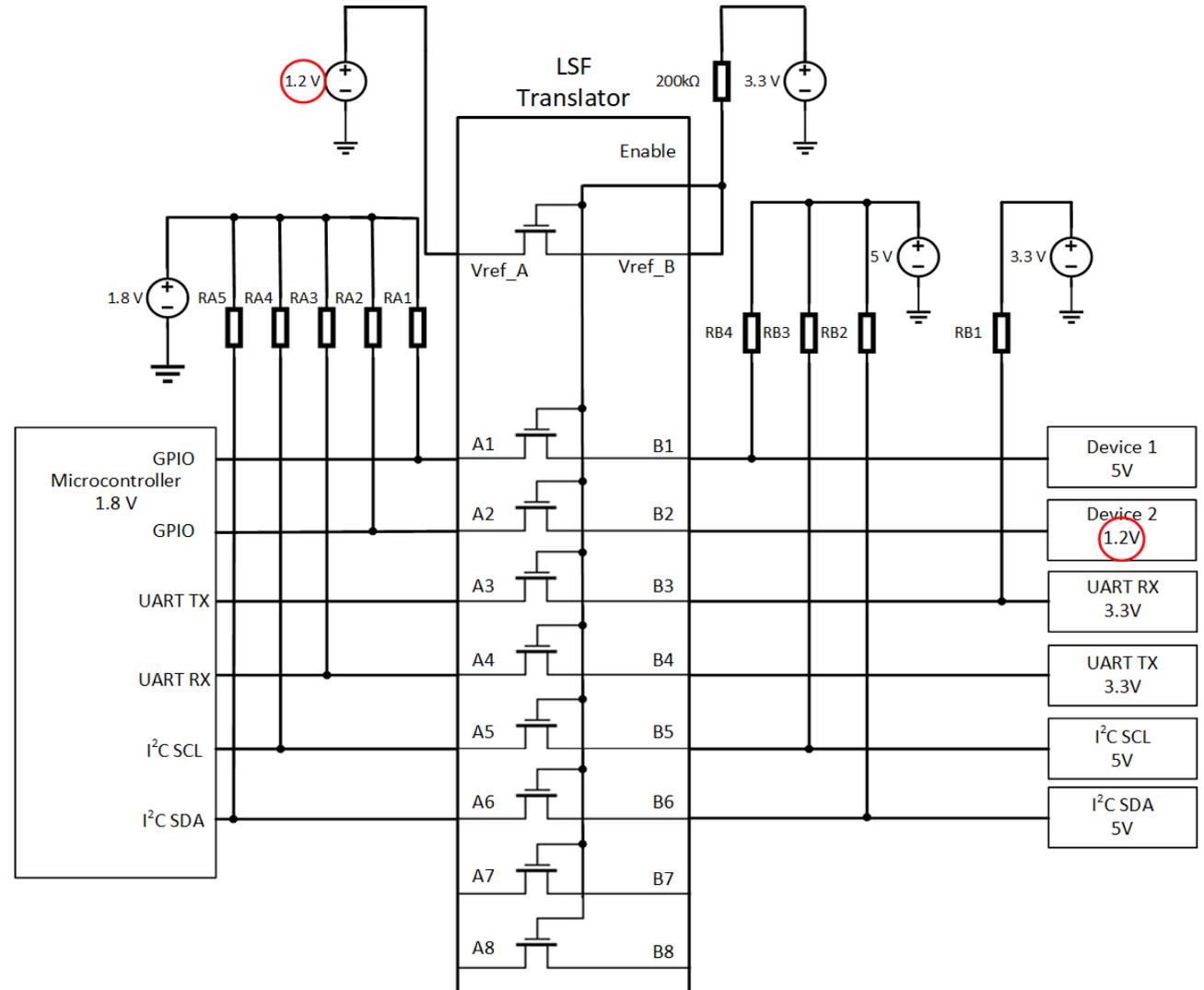- Various voltage levels:
 - Different voltage levels possible
 - Independent pull-up voltage configuration per channel
 - Vref_A must be the lowest voltage in the system
 - Supply of Device 2 is the same as Vref_A, therefore no pull-up needed for the receiver




Autosense translator LSF: Open-Drain vs. Push-Pull interfaces

- Scenario of a LSF translator with open-drain devices
- LSF has no driving capability => external pull-up Resistors are needed for transmitter and receiver
- Pull-up resistors can be calculated:


$$R_{PU} = \frac{V_{CC_B} + V_{CC_A} - 2V_{IL}}{I/O}$$

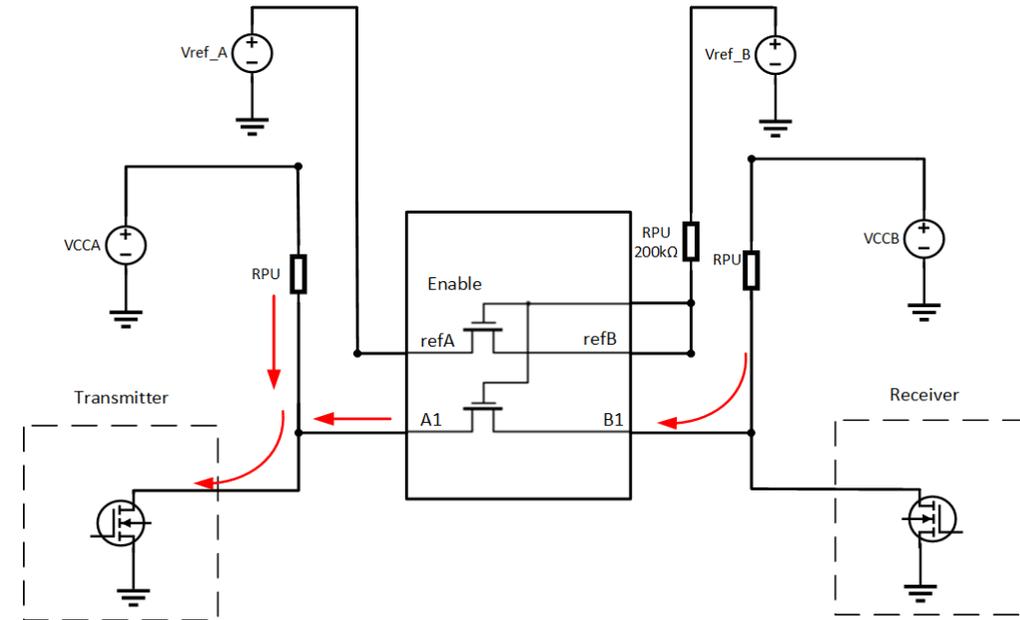- Typical value range is $\sim 0.6 - 4k\Omega$
- Maximum current scenario:
 - Transmitter is driving a low level
 - continuous current through the pass transistor
 - Current rate $\sim 1-8mA$




Autosense translator LSF: Push-Pull vs. open-drain interfaces

- Scenario of a LSF translator with push-pull participant
- LSF has no driving capability => an extra pull-up Resistor is needed at the input of the receiver
- In case of bidirectional data flow, a conflict can occur: both participants are driving, one is driving high, the other is driving low
 - A push-pull driver is driving with the high-side PMOS transistor, typically with R_{DSon} of $\sim 50-100\Omega$
 - Resulting in continuous current of $\sim 25-50\text{mA}$ per channel (recommended max is 64mA per channel, but the high current is inefficient and not desired)
- Best to have fixed direction when using LSF for push-pull devices

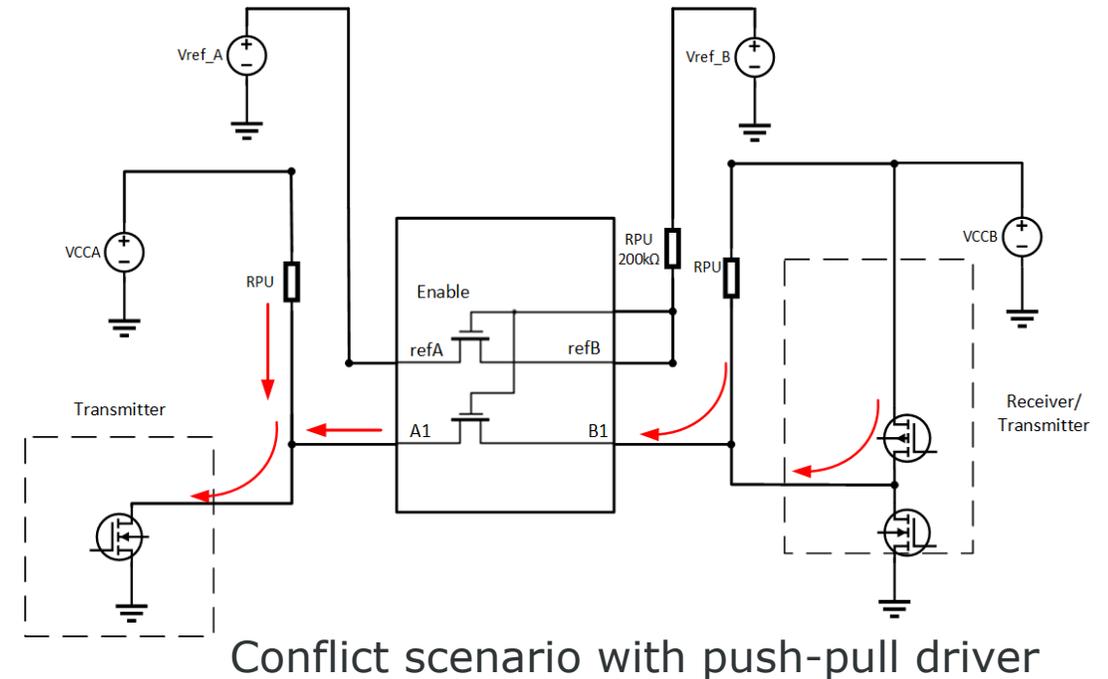

LSF pull-up supply case


- The reference channel is controlling the gate voltages for all translation channels
- Due to 200kΩ resistance between Enable and V_{ref_B}:
 - $V_{\text{Gate}} = V_{\text{ref_A}} + V_{\text{TH}}$
- Voltage source are assumed to be able to sink current if needed
- Simple voltage regulators (LDO) cannot sink current -> resulting in increased voltage at Vref_A
- The current flow can be estimated to
 - $(V_{\text{ref_B}} - V_{\text{ref_A}} - V_{\text{TH}}) / R_{\text{pu}} = 5\mu\text{A}$
- A possible workaround is a pull-down resistor at Vref_A
 - Resistor value = $V_{\text{ref_A}} / 5\mu\text{A} = 360\text{k}\Omega$

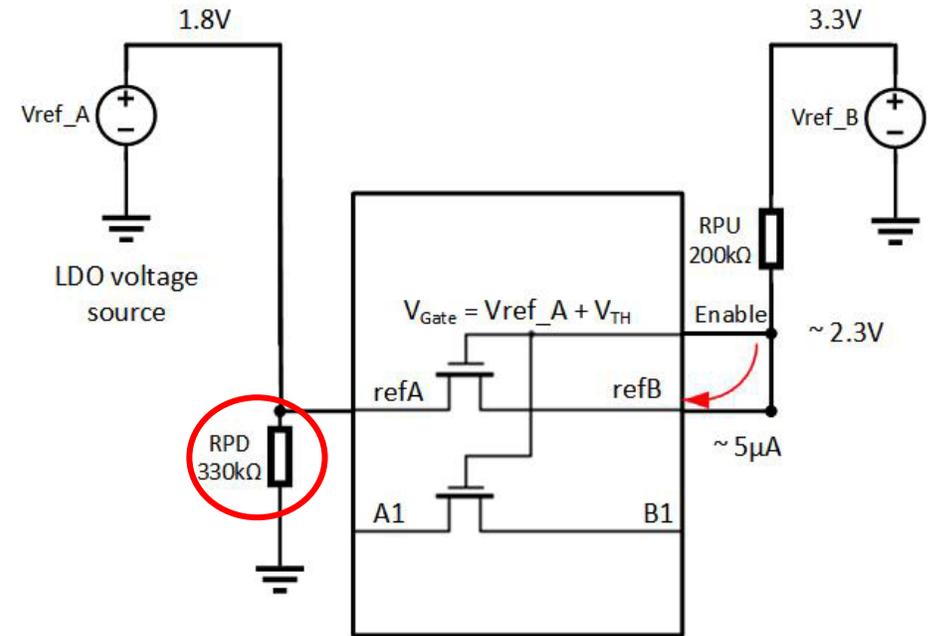

NXB with open drain receiver

- In steady state (high, low), only the buffer via 4K Ω is driving the load, one-shots are off!
- In case of external pull-up or pull-down resistor: Voltage divider network

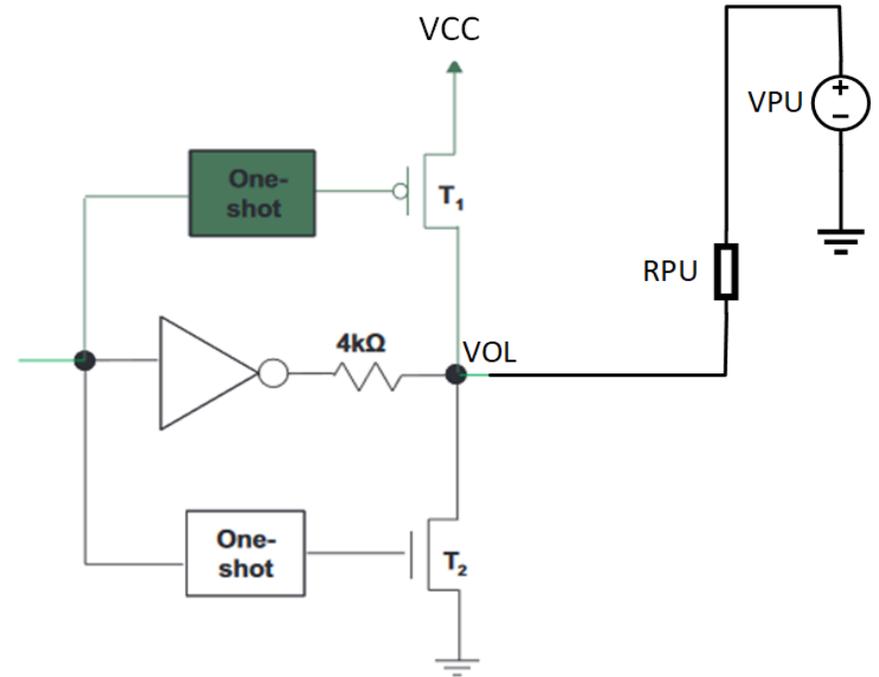- Pull-up:
$$V_{OL} = \frac{V_{PU} * 4k\Omega}{R_{PU} + 4k\Omega}$$




Voltage Translators | Support Material

Extensive information and support available on Nexperia.com

Leaflets




Youtube Videos

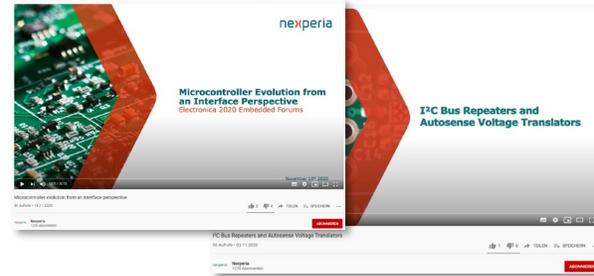


External webinars (recordings are available)

Logic Applications Handbook

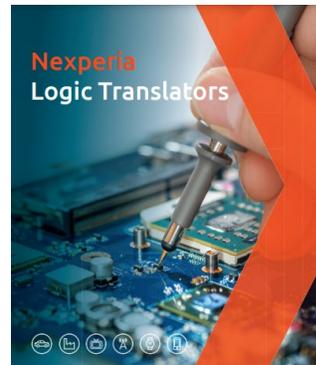

Translator Guide

nexperia
EFFICIENCY. VERSILY.

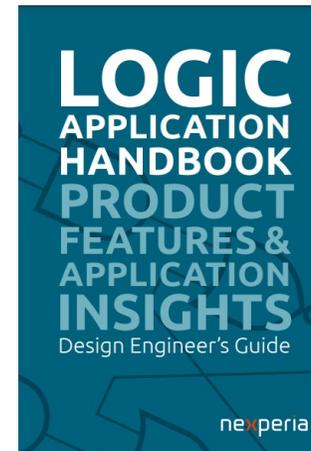

If you'd like to receive a free hardcopy of the Logic Application Handbook, please leave your shipping details in the questionnaire form after this webinar

Q&A